



ELEC 341 – Graded Assignments

## Project P-3

# 8 Marks
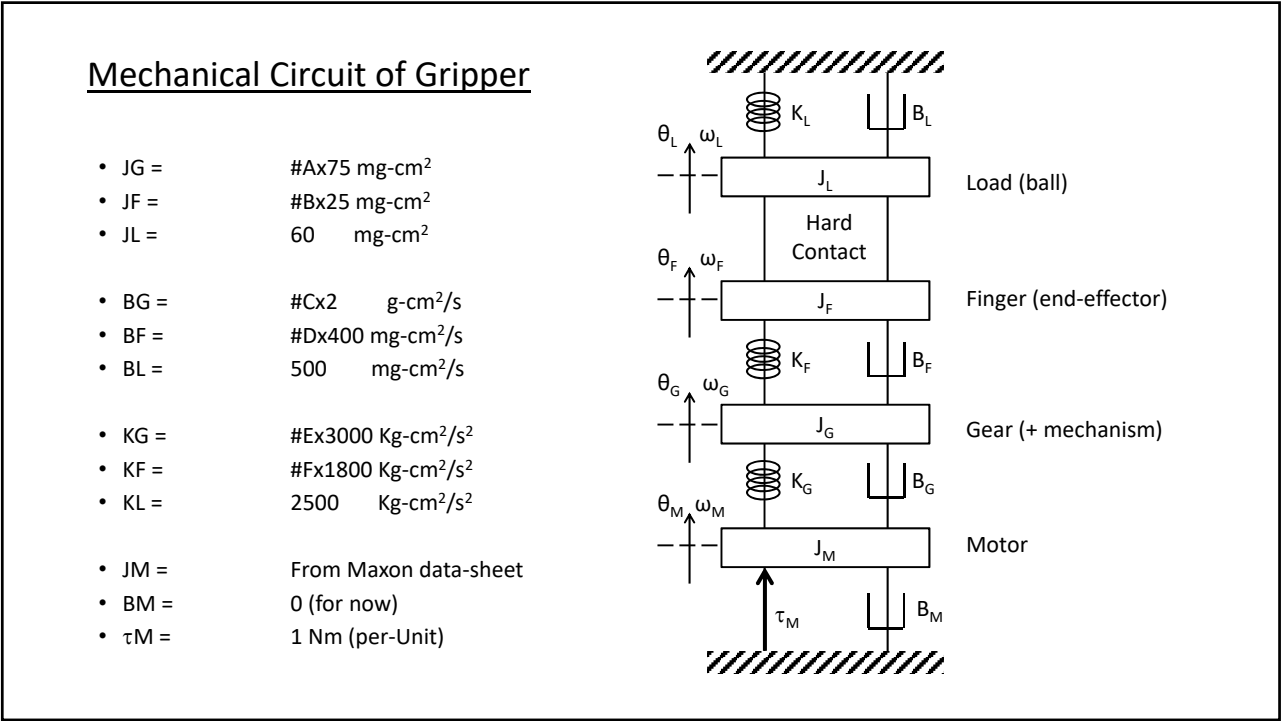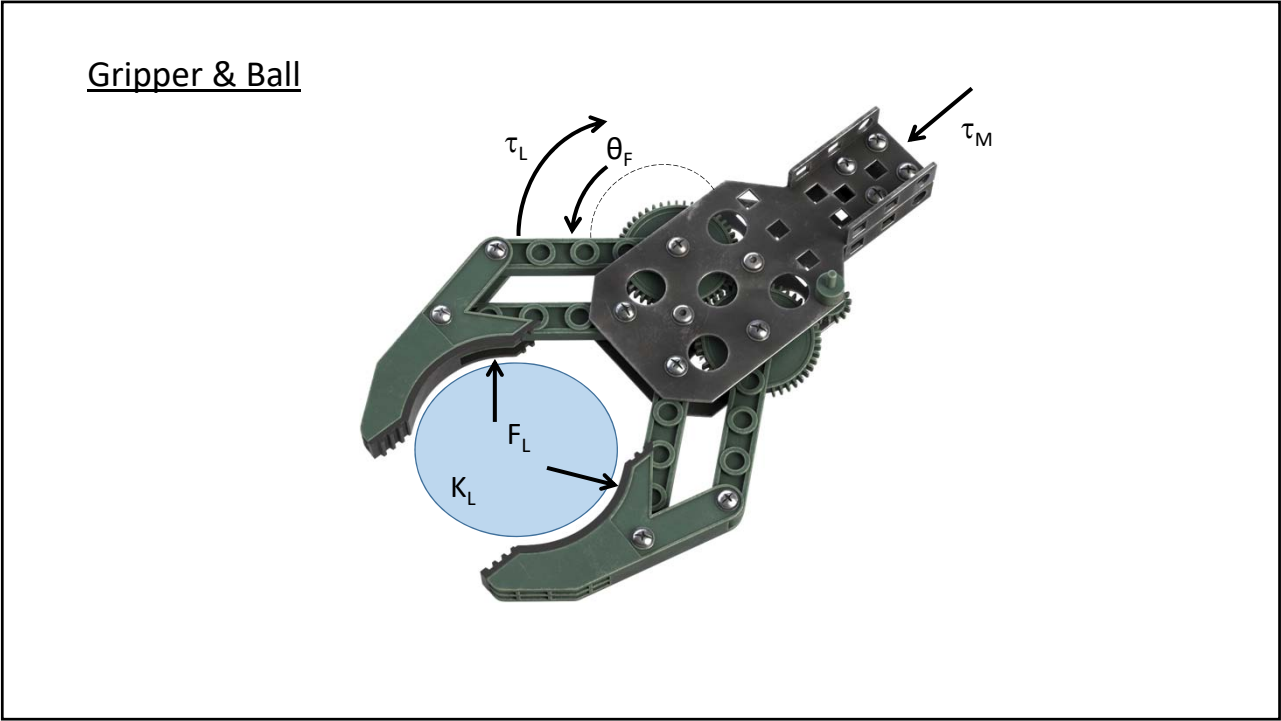
### Learning Objectives

- Using Nodal Analysis to Solve Transfer Function of Actuated Gripper
  - Simplified Motor Model
  - Motor Angle
  - Finger Angle



*A robot gripper is shown grasping a rubber ball. A simplified mechanical circuit representing the gripper and ball is also shown.*

*$\tau_M$  is the torque applied by the motor.*

*$F_L$  is the load force applied by the ball to the finger, as a result of the ball stiffness  $K_L$ .*

*Only half of the symmetrical gripper is included in the model for the sake of simplicity.*

### Equivalent Electric Circuit

Transform the Mechanical Circuit into an equivalent Electric Circuit.

- Draw the electric circuit
- Annotate it with component labels ( $R_1$ ,  $L_1$ ,  $C_1$ , etc.)

### Mechanical Y of Loaded Motor (with Gripper)

You are using the **12V** motor on **page (#A+70)** of the Maxon Catalog.

Use nodal analysis to compute the following transfer function.

Use **minreal()** to cancel any common factors.

- $P3\_Ym = \omega_M / \tau_M = \text{Motor Speed} / \text{Motor Torque (rad/Nms)}$

*Use the Maxon Motor catalog posted on Canvas. Use the 2020/2021 version.*

*Don't get a new copy from **maxongroup.com** because the page numbers are different.*

### Step Response

Generate the step response of the following angles.

Plot both on the same figure.

Apply a step with a torque that is  $\frac{1}{2}$  of the Stall Torque of your motor.

- $\theta_M$
- $\theta_L$
- All Angles (deg)
- Time (sec)

*Don't forget –  $Y_m$  delivers speed, not angle, for an applied torque.*

*Matlab has function called **dcgain()** which should match what you see on your plots.*

*Is there an easy way to make sure you are getting a realistic value ???*

*Consult your electric circuit and figure out how much DC current you expect. This is ball torque. How much should it be compressed to deliver this ???*

*Do the 2 plots vary much from one another ??? Is this what you expect ???*

*Consult the mechanical circuit and imagine what it would do if you built it exactly as shown and applied the force with your finger.*

<u>Deliverables</u>			
Values		Figures	
• P3_Ym	(3 marks)	• Equiv Elec CCT	(2 marks)
		• Step Responses	(3 marks)